

## **V = IR and Ohm's Law Worksheet**

In this worksheet, you will find some problems based on diagrams and others without diagrams. In all cases, show your work.

1. How much current is in a circuit that includes a 9-volt battery and a bulb with a resistance of 3 ohms?
2. How much current is in a circuit that includes a 9-volt battery and a bulb with a resistance of 12 ohms?
3. A circuit contains a 1.5 volt battery and a bulb with a resistance of 3 ohms. Calculate the current.
4. A circuit contains two 1.5 volt batteries and a bulb with a resistance of 3 ohms. Calculate the current.
5. What is the voltage of a circuit with 15 amps of current and toaster with 8 ohms of resistance?
6. A light bulb has a resistance of 4 ohms and a current of 2 A. What is the voltage across the bulb?
7. How much voltage would be necessary to generate 10 amps of current in a circuit that has 5 ohms of resistance?
8. How many ohms of resistance must be present in a circuit that has 120 volts and a current of 10 amps?
9. An alarm clock draws 0.5 A of current when connected to a 120 volt circuit. Calculate its resistance.
10. A portable CD player uses two 1.5 V batteries. If the current in the CD player is 2 A, what is its resistance?
11. You have a large flashlight that takes 4 D-cell batteries. If the current in the flashlight is 2 amps, what is the resistance of the light bulb? (Hint: A D-cell battery has 1.5 volts.)
  
12. Use the diagram below to answer the following problems.